

Department of Electronics Academic Year: 2023-24

BVLSI Course Project Report

Title of Project - Program Counter


Mentor - Mr. Yogesh Pandit

Group Number	Name	Roll Number
5	Vansh Dhoka	5
	Atharva Godkar	31
	Anish Godse	32
	Sukanya Pingle	47

Introduction -


Program Counter is very important part of any microprocessor or microcontroller. Its job is the store the address of next instruction to be executed. It is basically a combination of up counter and PIPO register. For general instruction, PC simply increase the count by 1 after every instruction gets executed. For Branch instructions the PC directly loads the address of next instruction to be executed. These are the 2 modes of operation of a PC. These 2 modes are selected using 2 control signals i.e increment & load. We have used cadence virtuoso tool to design PC. We have adopted **bottom to top design methodology** for completing this project. For eg. We first built 1bit adder, followed by 4bit adder, and then finally complete PC. We have **Transmission Gate design style** for making PC. We are making 4 bit PC (range = 0 to 15).


Circuit Diagram -

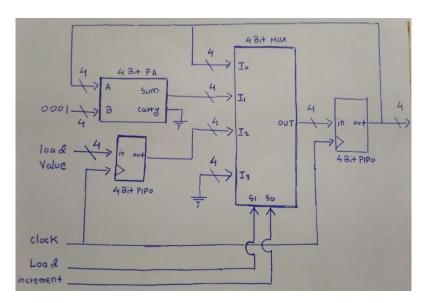



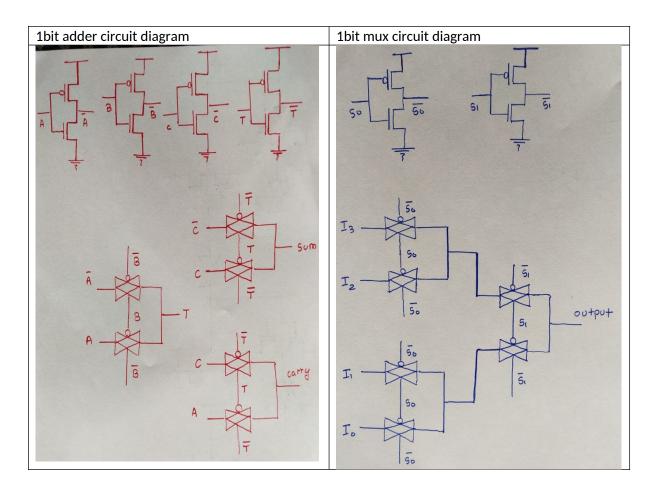Department of Electronics Academic Year: 2023-24




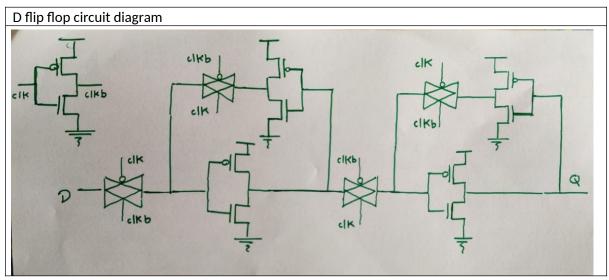



Digital circuit	Transmission gate style	Static CMOS style
1 bit adder	20 MOSFETS	46 MOSFETS
1bit mux	16 MOSFETS	70 MOSFETS
D flip flop	18 MOSFETS	18 MOSFETS


Department of Electronics Academic Year: 2023-24

Result & Conclusion -

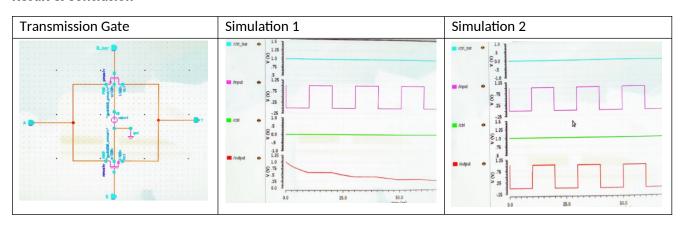

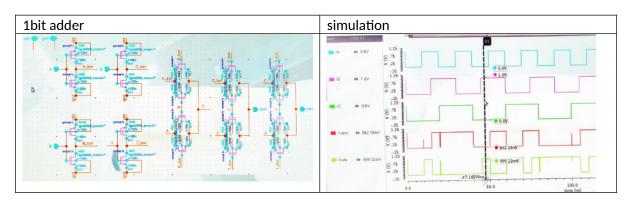


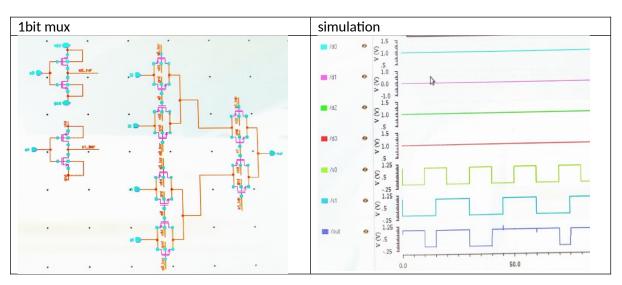


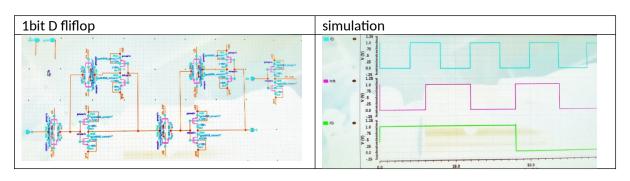




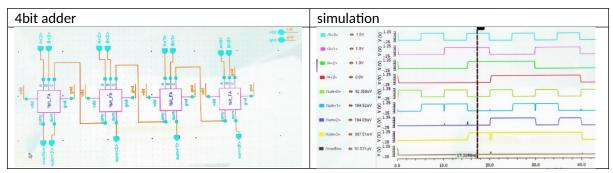Department of Electronics Academic Year: 2023-24




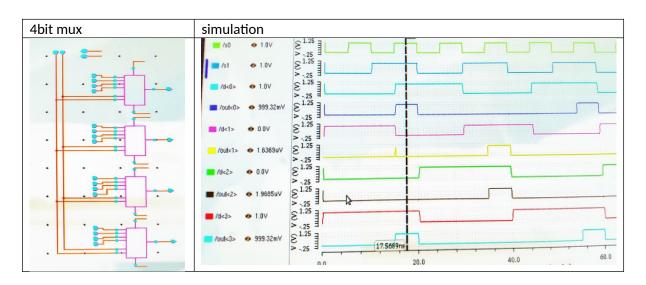

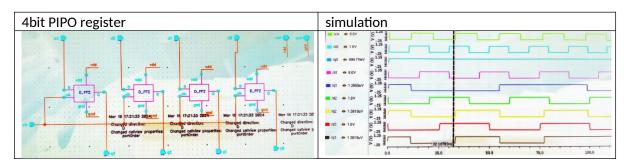


Department of Electronics Academic Year: 2023-24

4bit program counter

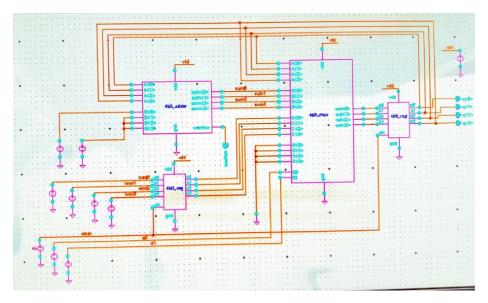

Simulation when load = 1 & increment = 0

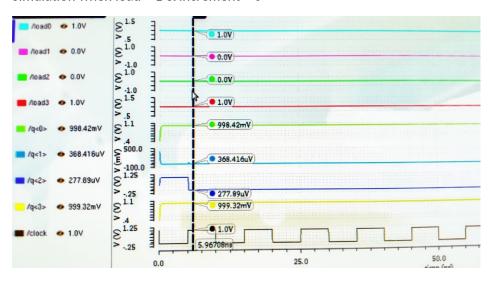

Simulation when load = 0 & increment = 1

